

Ag2120 / Ag2130 Parallel Phone and Line Detect Circuit



This circuit will work with either an Ag2120 or Ag2130, $V_{CC} = 3.3V$ or $5.0V$.

The circuit only requires 1 x quad comparator, 1 x quad 10K resistor network, 2 x 390R resistors, 2 x 100R resistors and 1 x 100nF capacitor (all resistors tolerances are $\pm 1\%$).

V_{REF} is used as the reference and V_{TR} equals the voltage across TIP & RING divided by 220 (with respect to V_{REF}).

Table 1 shows the output logic states for the different line conditions.

| Line Conditions | PPhone | LStatus |
|------------------------------------------------|--------|---------|
| Line detected and parallel phone is ON-Hook | 0 | 0 |
| Line detected and parallel phone is OFF-Hook * | 1 | 0 |
| No line detected | 1 | 1 |

Table 1

* This state also applies if the Ag2120 or Ag2130 goes OFF-Hook (LSC = 1)

